



UNIVERSITY EXAMINATIONS

EXAMINATION FOR JANUARY/APRIL 2015/2016 FOR BACHELOR OF SCIENCE IN COMPUTER SCIENCE

RCCS 101: - DIGITAL LOGIC.

DATE: 13th/April /2016.

TIME: 2 HOURS

GENERAL INSTRUCTIONS:

Students are NOT permitted to write on the examination paper during reading time.

This is a closed book examination. Text book/Reference books/notes are not permitted.

SPECIAL INSTRUCTIONS:

This examination paper consists Questions in Section A followed by section B.

Answer **Question 1 and any Other Two** questions.

QUESTIONS in ALL Sections should be answered in answer booklet(s).

1. **PLEASE start the answer to EACH question on a NEW PAGE. You will lose 5 MARKS if this is not done.**
2. **Keep your phone(s) switched off at the front of the examination room and NOT on your person.**
3. **Keep ALL bags and caps at the front of the examination room and DO NOT refer to ANY unauthorized material before or during the course of the examination.**
4. **ALWAYS show your working.**
5. **Marks indicated in parenthesis i.e. () will be awarded for clear and logical answers.**
6. **Write your REGISTRATION No. clearly on the answer booklet(s).**
7. **For the Questions, write the number of the question on the answer booklet(s) in the order you answered them.**
8. **Calculator will be required.**

SECTION A (COMPULSORY)

Question (1) - (30Marks)

a) Differentiate between Analog and Digital Signals. **(2 Marks)**


b) With respect to digital electronics circuits signals, define the following terms. **(5Marks)**

- i. Rise time.
- ii. Fall time.
- iii. Propagation time.
- iv. Fan out.
- v. Fan in.

c) Implement the Boolean expression below using suitable logic gates.

$$Y_{\text{out}} = [(AB) C + (CDE) (BCE)]. \quad \textbf{(5 Marks)}$$

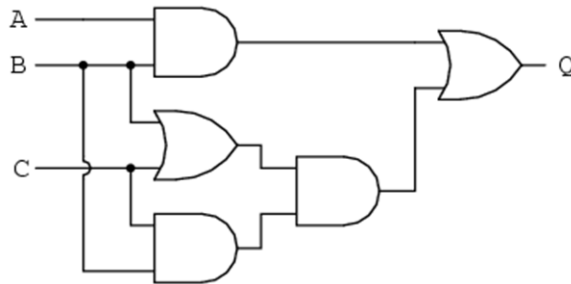d) Considering the digital circuit below, derive the Boolean function (Q) that is an equivalent expression of the circuit. **(5 Marks)**



e) Work out the following calculations. (Show the working) **(6 Marks)**

- i. $11111111_2 + 456_8$ Results in decimal number.
- ii. $BACB_{16} + 111001100011_2$ Results in decimal number.
- iii. $1357_8 + 9BDF_{16}$ Results in Hexadecimal number.

f) Describe the functions of the ADC and DAC in the digital and computer system. Hence give two types of ADC circuitry. **(4 Marks)**

g) Define the De-Morgan's theorem, and show both variations of it. **(3 Marks)**

SECTION B (Answer Any Two Questions)

Question (2) - (20Marks)

- a) Express the following numbers in the specified Format. **(4 Marks)**
- 10101001_{binary} - into Gray Code.
 - 11010101_{gray} - into Binary.
 - 111001011001_2 - Octal number.
 - 111101010101_2 - Two's complements.
- b) Perform the following calculations. **(8 Marks)**
- $1111_2 - 7_{10}$ - Using twos complements.
 - $AFDE_{16} + 79CDF_{16}$ - Express the results in Hexadecimal.
 - $10111011_2 + 10110111_2$ - Express the results in Decimal.
 - $1010_2 \times 1111_2$ - Express the results in Decimal.
- c) Name two universal gates used in the digital circuitry fabrication. **(2 Marks)**
- d) Using any universal gate of your choice, implement the following basic logic gates.
- NOT Gate. **(1 Marks)**
 - AND Gate. **(2 Marks)**
 - OR Gate. **(3 Marks)**

Question (3) - (20Marks)

- a) State uses of the Gray code in digital electronics/communication. **(2 Marks)**
- b) Design a four bit Binary to gray code converter circuit. NB you can use the K-Mapping method or the Boolean simplification method. Hence implement the logic circuit. **(12 Marks)**
- c) Describe the functionalities of the following digital circuits. **(6Marks)**
- Flip flop.
 - Counters.
 - Multiplexers.
 - De-multiplexers.
 - Memory cell.
 - Encoders

Question (4) - (20Marks)

- a) Using **Karnaugh Mapping** technique of Boolean simplification, simplify the Boolean function below to the simplest term. **(8 Marks)**

$$Y_{out} = \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + \overline{A}B\overline{C}D + \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + \overline{A}B\overline{C}D + \overline{A}B\overline{C}D + \overline{A}B\overline{C}\overline{D}$$


- b) Draw the basic logic gates, used in Digital electronics. Hence show their truth tables as well as the Boolean expressions. **(7 Marks)**

- c) Convert the following numbers, into the indicate number systems. **(5Marks)**

- i. 135_{10} into binary number.
- ii. 2460_8 into decimal number.
- iii. 11000011_2 into decimal number.
- iv. $DAABC00_{16}$ into octal number.
- v. 10101111110101100010_2 into Hexadecimal number.

Question (5) - (20Marks)

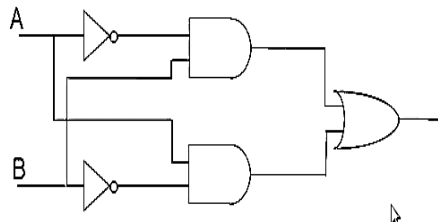- a) Differentiate between a full adder and half adder. **(4 Marks)**
(Use suitable block diagram)
- b) Design a full adder circuit, and implement the circuit using suitable gates. **(8 Marks)**
- c) Simplify the following digital circuit to the simplest circuit. **(3 Marks)**



- d) Select the collect choice, in the following multiple choice questions. **(5 Marks)**

- i. How many JK - Flip-Flops are required for mod-64 counter?
(A) 5.
(B) 6.
(C) 8.
(D) 4.

- ii. What is the binary equivalent of the decimal number 368?
 - (A) 101110000.
 - (B) 110110000.
 - (C) 111010000.
 - (D) 111100000.

- iii. In which of the following gates, the output is 1, if at least one input is 1
 - (A) NOR.
 - (B) AND.
 - (C) OR.
 - (D) NAND.

- iv. The time required for a gate to change state is referred to as
 - (A) Fall time.
 - (B) Decay time.
 - (C) Propagation time.
 - (D) Rise time.

- v. Which of the following gates can be used in detecting Parity bits in error correction
 - (A) OR gate.
 - (B) AND gate.
 - (C) NOR gate.
 - (D) XOR gate.