



**UNIVERSITY EXAMINATIONS**

**EXAMINATION FOR SEPTEMBER/DECEMBER 2019/2020 FOR BACHELOR OF  
SCIENCE IN COMPUTER SCIENCE**

**RCS 101: DIGITAL LOGICS.**

**DATE: 11<sup>TH</sup> DECEMBER 2019**

**TIME: 2 HOURS**

**GENERAL INSTRUCTIONS:**

Students are NOT permitted to write on the examination paper during examination time.

This is a closed book examination. Text book/Reference books/notes are not permitted.

**SPECIAL INSTRUCTIONS:**

This examination paper consists Questions in Section A followed by section B.

Answer **Question 1 and any Other Two** questions.

QUESTIONS in ALL Sections should be answered in answer booklet(s).

1. **PLEASE start the answer to EACH question on a NEW PAGE.**
2. **Keep your phone(s) switched off at the front of the examination room.**
3. **Keep ALL bags and caps at the front of the examination room and DO NOT refer to ANY unauthorized material before or during the course of the examination.**
4. **ALWAYS show your working.**
5. **Marks indicated in parenthesis i.e. ( ) will be awarded for clear and logical answers.**
6. **Write your REGISTRATION No. clearly on the answer booklet(s).**
7. **For the Questions, write the number of the question on the answer booklet(s) in the order you answered them.**
8. **Calculator will be required, DO NOT use your PHONE as a CALCULATOR.**
9. **YOU are ONLY ALLOWED to leave the exam room 30minutes to the end of the Exam.**
10. **DO NOT write on the QUESTION PAPER. Use the back of your BOOKLET for any calculations or rough work.**
11. **Calculator will be required.**

## SECTION A (COMPULSORY)


### Question (1) - (30Marks)

- a) Define the following terminologies as used in digital logics. **(5 Marks)**
- Bit.
  - Byte.
  - Parity.
  - Nibble.
  - Overflow.
- b) The modern computers are able to process both digital and analog signals/data, discuss how that is achieved. **(4 Marks)**
- c) Describe the following digital logic circuits and state how they are used in computers. **(5 Marks)**
- Encoder.
  - Decoders.
  - Flip – Flops.
  - Multiplexers.
  - De-Multiplexers.
- d) List **FOUR** Number systems used in digital electronics, state their bases and showing all character ranges. **(4 Marks)**
- e) Evaluate the following Conversions for the following numbers, into the indicate format. Show all the working. **(10 Marks)**
- $10101011001101_2$  into Hexadecimal number.
  - $10101010101010_{bin}$  into Gray code.
  - $101010101_2$  into decimal number.
  - $ABC0_{16}$  into octal number.
  - $157_{10}$  into binary number.
- f) What are the universal logic gates? Give examples. **(2 Marks)**

## SECTION B (Answer Any Two Questions)

### Question (2) - (20Marks)

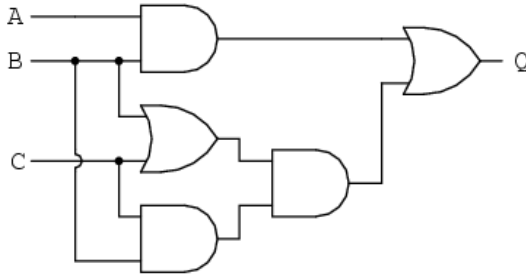- a) State and prove the De-Morgan's theorem. You can use truth table. **(6 Marks)**
- b) Considering the logic circuit below.




- i. Derive its output function (Q). **(3 Marks)**
  - ii. Simplify the function to its simplest form. **(4 Marks)**
  - iii. Draw the logic circuit for the simplified function. **(3 Marks)**
- c) With reference to Analog to Digital Converters (ADC) and Digital to Analog Converters (DAC) discuss the concept of DSP (Digital Signal Processing). **(4 Marks)**

### Question (3) - (20Marks)

- a) Discuss the following level of integration scales as used in Digital Integrated Chips (ICs) fabrication. **(5 Marks)**
- i. Small Scale Integration (S.S.I).
  - ii. Medium Scale Integration (M.S.I).
  - iii. Large Scale Integration (L.S.I).
  - iv. Very Large Scale Integration (V.L.S.I).
  - v. Ultra Large Scale Integration. (U.L.S.I).
- b) Perform the following conversions. **(6 Marks)**
- i.  $1011010.101011_{\text{bin}}$  - to decimal format.
  - ii.  $135.245_{\text{dec}}$  - to binary format.
- c) Considering the boolean logic function below.
- $$Y_o = \{\bar{A}BC + A\bar{B}C + ABC\bar{C} + ABC\}$$
- i. Draw an equivalent digital circuit. **(4 Marks)**
  - ii. Simplify the function to have lowest number of gates. **(5 Marks)**

### Question (4) - (20Marks)

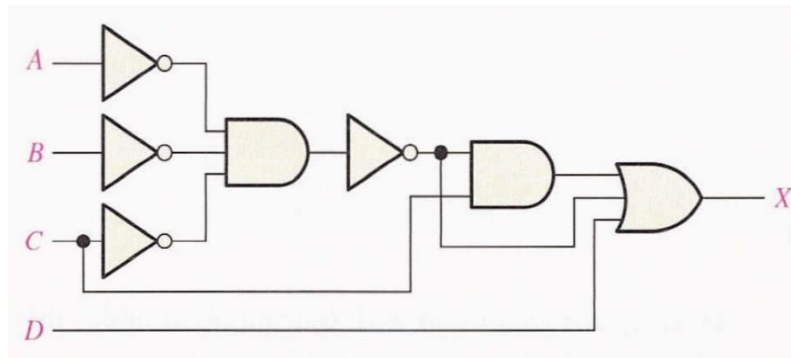- a) Describe the following terms as used in digital circuits. (5 Marks)
- i. Propagation Delay.
  - ii. Fall Time.
  - iii. Rise time.
  - iv. Fan Out.
  - v. Fan In.
- b) Derive the output function ( $X$ ) for the Combination circuit below. (5 Marks)



- c) Draw five basic logic gates, used in digital designs and derive the *Truth tables* and *Boolean functions*. (10 Marks)

### Question (5) - (20Marks)

- a) Using Karnaugh-Mapping, design a **four bits - binary to gray** code converter and implement the logic circuit. (10 Marks)
- b) Simplify the boolean expression illustrated below. (4 Marks)

$$X = (\overline{\overline{A}\overline{B}\overline{C}})C + \overline{\overline{A}\overline{B}\overline{C}} + D$$

- c) Explain how the Successive-Approximation, Analog to Digital Converter function/operates. (4 Marks)
- d) Differentiate between the combinational and sequential logic circuits. (2 Marks)

END